

# Unit 8. Ordinary Differential Equations

Numerical Analysis

May 26, 2015

## Introduction

- In this unit, we are solving the ordinary differential equation (ODE)


$$\frac{dx}{dt} = f(t, x), \quad (8.1.1)$$

where  $x$  is a function of  $t$  and with the conditions  $t \in [t_0, t_f]$  and  $x(t_0) = x_0$ .

- $t_f$  can approach infinite.
- Since the value of  $x_0$  needs to be known and we solve for  $t > t_0$ , this type of problems is also known as **initial value problem** (IVP).
- Problems of this type are abundant in our world.
  - In SPICE, this is the transient analysis.
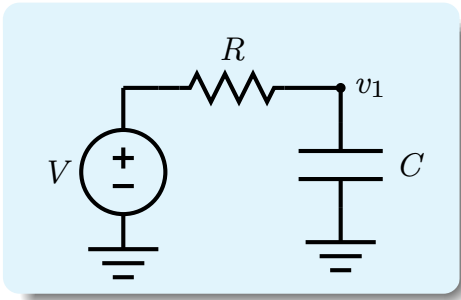
# Simple RC Circuit

- A simple example, to solve for the RC network with



$$V(t) = 1, \quad t \geq 0,$$

$$v_1(0) = 0.$$

- Analytical solution

$$v_1(t) = 1 - \exp\left(-\frac{t}{RC}\right).$$

- Nodal analysis at node  $v_1$  (KCL)

$$\frac{V - v_1}{R} + C \frac{dv_1}{dt} = 0.$$

- Or

$$\frac{dv_1}{dt} = \frac{V - v_1}{RC}. \quad (8.1.2)$$

- This equation has the same form as Eq. (8.1.1), with  $x = v_1$  and  $f(x, t) = (V - v_1)/RC$ .
  - Note that  $f$  depends on  $x$  as well, and  $t$  is implicit.
  - In some applications,  $f$  can be explicit function of  $t$  as well.

## Simple RC Circuit, II

- Assuming  $v_1$  is differentiable,

$$\frac{dv_1}{dt} = \frac{v_1(t+h) - v_1(t)}{h} \quad \text{as } h \rightarrow 0.$$

- Substitute into Eq. (8.1.2),

$$\begin{aligned} \frac{v_1(t+h) - v_1(t)}{h} &= \frac{V(t) - v_1(t)}{RC} \\ v_1(t+h) &= v_1(t) + h \cdot \frac{V(t) - v_1(t)}{RC} \end{aligned}$$

- Giving  $V(t)$ ,  $t \geq 0$ , and  $v_1(0)$  then we can find  $v_1(t)$ ,  $t \geq 0$ .



- Let  $y = \frac{h}{RC}$  then

$$v_1(t+h) = (1 - y)v_1(t) + y \cdot V(t) \quad (8.1.3)$$

- And

$$\begin{aligned} v_1(0) &= 0, \\ v_1(h) &= y, \\ v_1(2h) &= (1 - y)y + y = (2 - y)y, \\ v_1(3h) &= (1 - y)(2 - y)y + y = (3 - 3y + y^2)y, \\ &\dots \end{aligned}$$

# Forward Euler Method

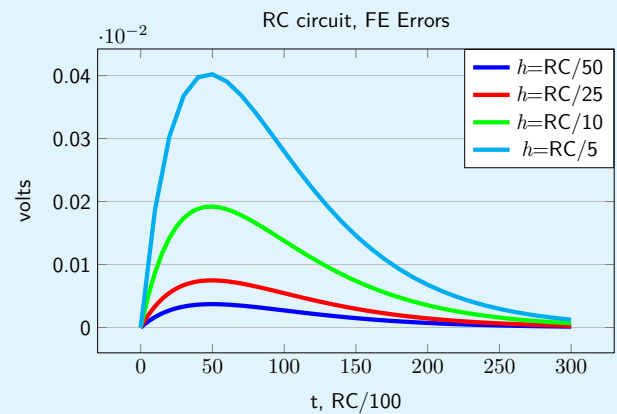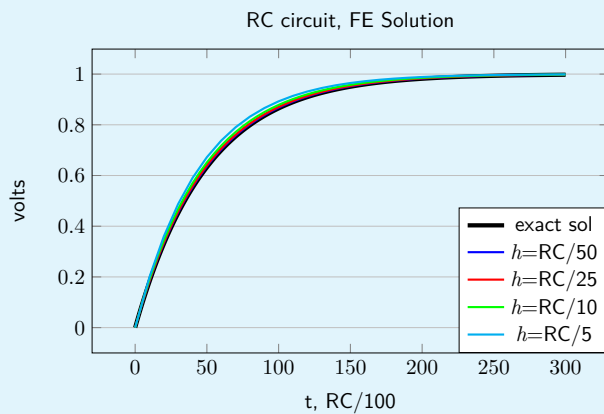



- In general, Eq. (8.1.1) can be solved by

$$x(t+h) = x(t) + h \cdot f(t) \quad (8.1.4)$$

This is the **Forward Euler method**.

- For the simple RC network example, it can be observed that the Forward Euler method produces accurate solution.
  - even for relative large  $h$ .
- Of course, smaller  $h$  produces more accurate solution.

## Forward Euler Method, II

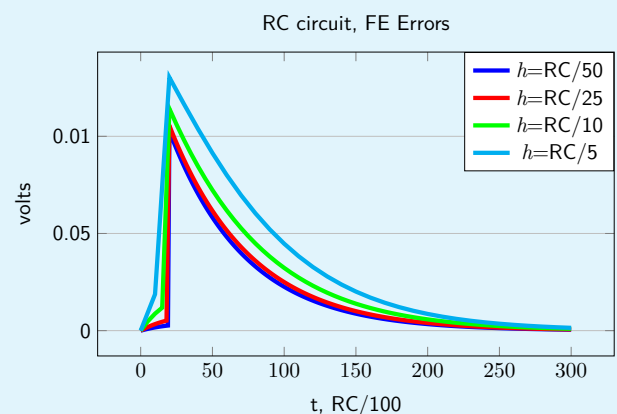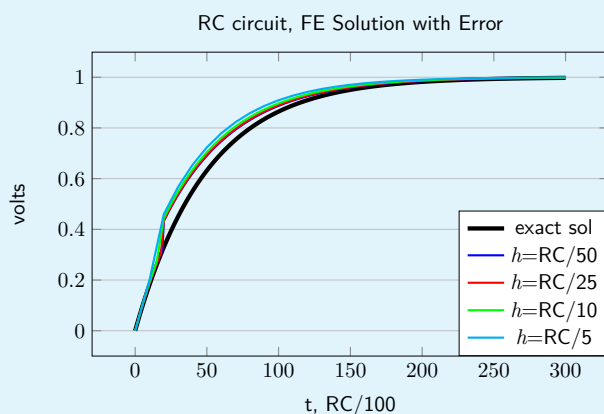

- An error is intentionally inserted at  $t = 0.2 \cdot RC$  when carrying out Forward Euler method.
- The error gradually decreases as  $t$  increases
- Error does not accumulated in Forward Euler method.
- If the initial solution, or the solution at any time point, is erroneous, the solution for large  $t$  can still be accurate.
- Error damping is also a function of  $h$ .

# Backward Euler Method

- Equation (8.1.1) can also be solved using the following equation.

$$\frac{x(t+h) - x(t)}{h} = f(t+h, x(t+h)).$$

And, hence

$$x(t+h) = x(t) + h \cdot f(t+h, x(t+h)). \quad (8.1.5)$$

- This is the **Backward Euler method**.
- The solution to the simple RC circuit can be written as

$$\begin{aligned} v_1(t+h) &= v_1(t) + h \cdot \frac{V(t+h) - v_1(t+h)}{RC} \\ (1 + \frac{h}{RC})v_1(t+h) &= v_1(t) + \frac{h}{RC} V(t+h) \end{aligned}$$



Let  $y = \frac{h}{RC}$  then

$$v_1(t+h) = \frac{1}{1+y} v_1(t) + \frac{y}{1+y} V(t+h). \quad (8.1.6)$$
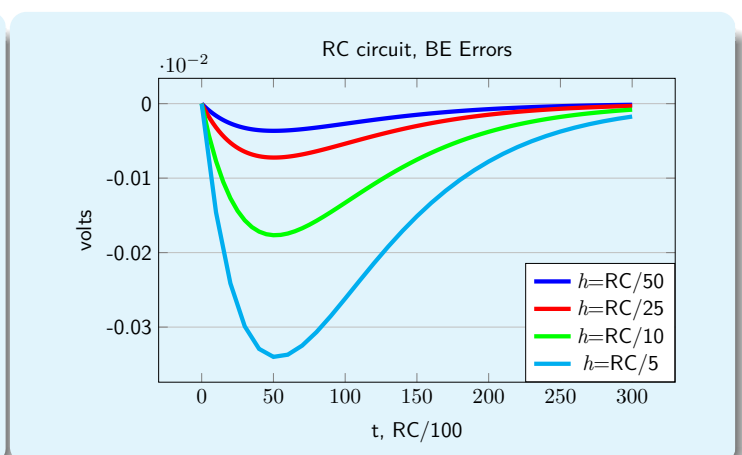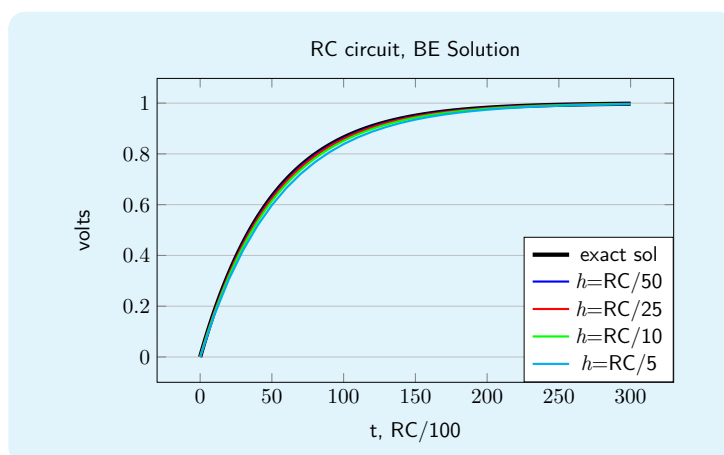
## Backward Euler Method, II



- And

$$\begin{aligned} v_1(0) &= 0 \\ v_1(h) &= \frac{y}{1+y} \\ v_1(2h) &= \frac{y}{1+y} \left( \frac{1}{1+y} + 1 \right) \\ v_1(3h) &= \frac{y}{1+y} \left( \frac{1}{(1+y)^2} + \frac{1}{1+y} + 1 \right) \\ &\dots \end{aligned}$$






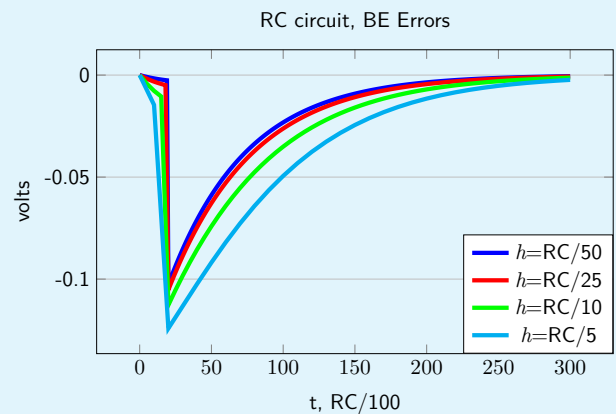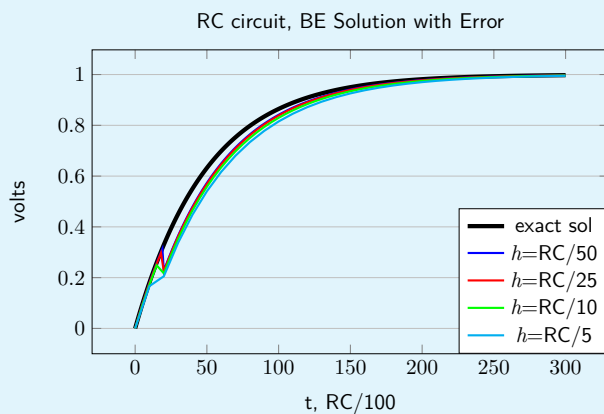
# Backward Euler Method, III

- Backward Euler method produces accurate results as well
- Even an error of  $-0.1$  volts is introduced intentionally at  $t = 0.2RC$
- Error damps out - no error accumulation
- Backward Euler method appears to be a little more accurate than Forward Euler method.



# Backward Euler Method, III

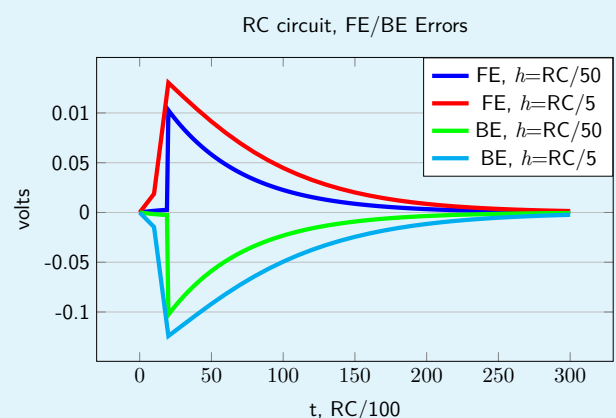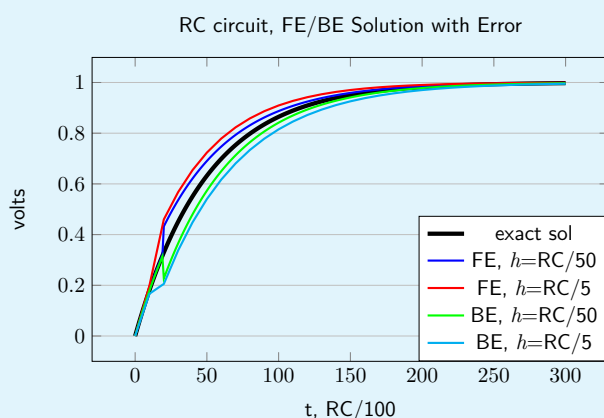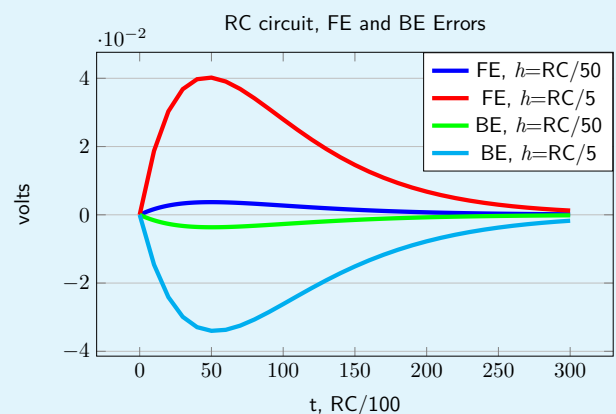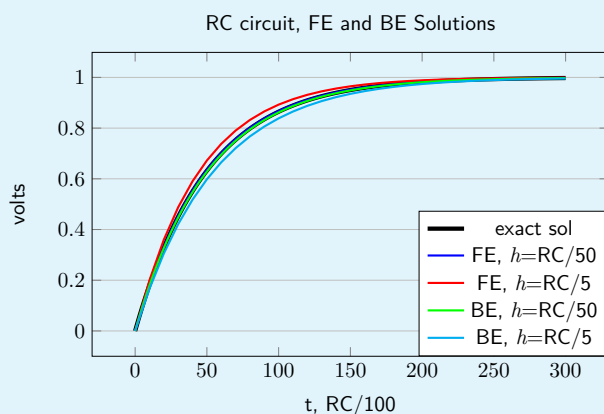

# First Order Solution Methods

- To solve the ordinary differential equation

$$\frac{dx(t)}{dt} = f(t)$$

- Forward Euler method

$$\frac{x(t+h) - x(t)}{h} = f(t)$$

- Backward Euler method



$$\frac{x(t+h) - x(t)}{h} = f(t+h)$$

- In the simple RC circuit example, these two methods do not make much difference.
- Let the voltage source waveform of the simple RC circuit be

$$V(t) = \begin{cases} t/RC, & 0 \leq t \leq RC, \\ 1, & t \geq RC. \end{cases}$$

- Forward Euler:  $v_1(t+h) = (1-y)v_1(t) + yV(t)$ .
- Backward Euler:  $v_1(t+h) = (v_1(t) + yV(t+h))/(1+y)$ .
  - $y = h/RC$ .

## First Order Solution Methods, II

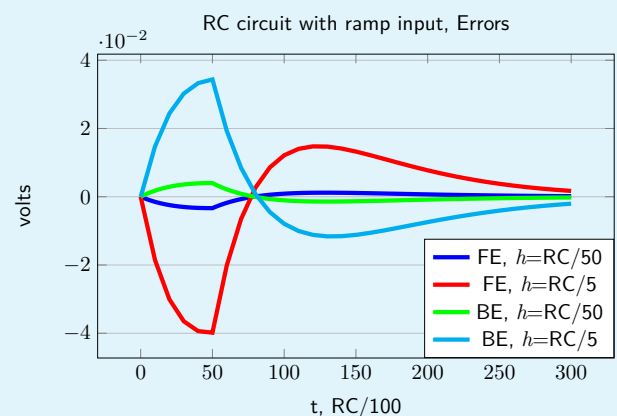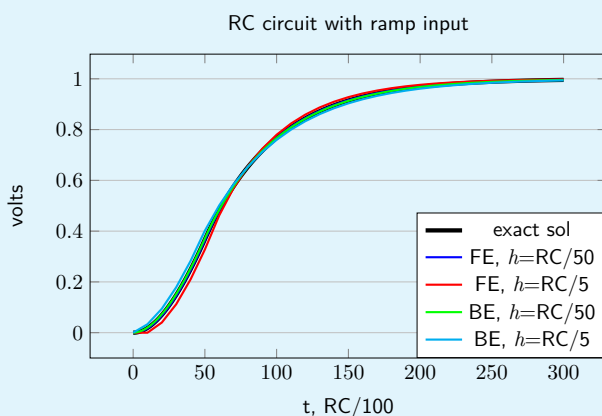

- Both methods produce accurate solutions.
- Backward Euler appears to be more accurate.
- Any input voltages can be solved.
- No error accumulation.
- Good accuracy even with relative large time steps.

# Trapezoidal Rule

- To solve the ODE

$$\frac{dx(t)}{dt} = f(x(t), t)$$

Note that

$$x(t) = x(t_0) + \int_{t=t_0}^t f(x(\tau), \tau) d\tau$$

- Both Forward Euler and Backward Euler methods are composite integration formula with zero'th order quadrature
- Trapezoidal rule can be more accurate and it is expressed as

$$x(t) = x(t_0) + h \cdot \frac{f(x(t+h), t+h) + f(x(t), t)}{2}.$$

- For the RC network

$$\frac{dv_1}{dt} = \frac{V(t) - v_1(t)}{RC}$$

Thus,



$$v_1(t+h) = v_1(t) + h \cdot \frac{V(t+h) - v_1(t+h) + V(t) - v_1(t)}{2RC}$$

## Trapezoidal Rule, II

- Let  $y = \frac{h}{RC}$ , then



$$(1 + 0.5y)v_1(t+h) = (1 - 0.5y)v_1(t) + 0.5y(V(t+h) + V(t))$$
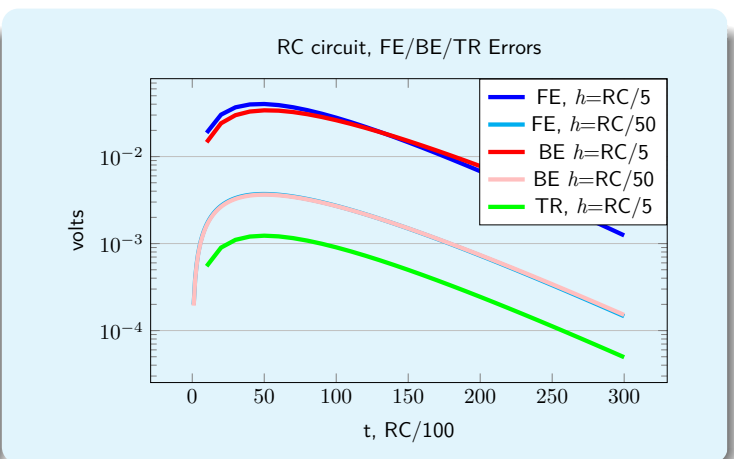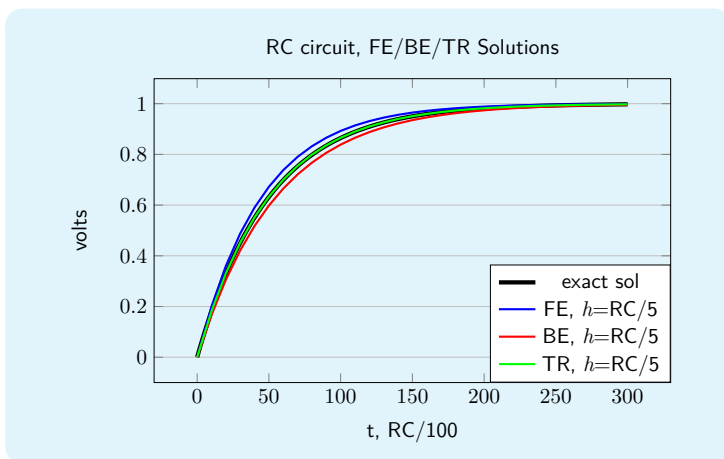
$$v_1(t+h) = \frac{1 - 0.5y}{1 + 0.5y}v_1(t) + \frac{0.5y}{1 + 0.5y}(V(t+h) + V(t))$$



- For RC network with step input, trapezoidal method with large time step is very accurate.
  - More accurate than Forward Euler or Backward Euler with 10 times small time step.

# Trapezoidal Rule, III

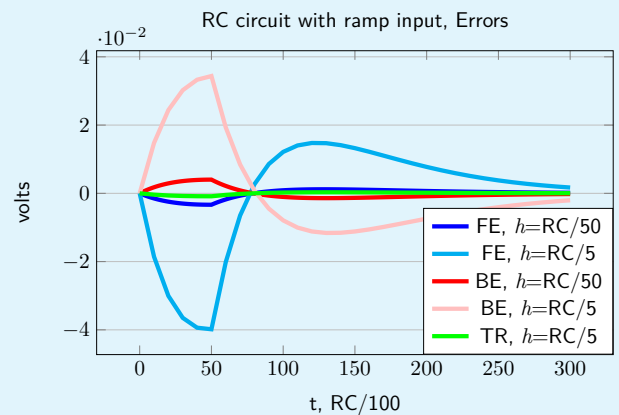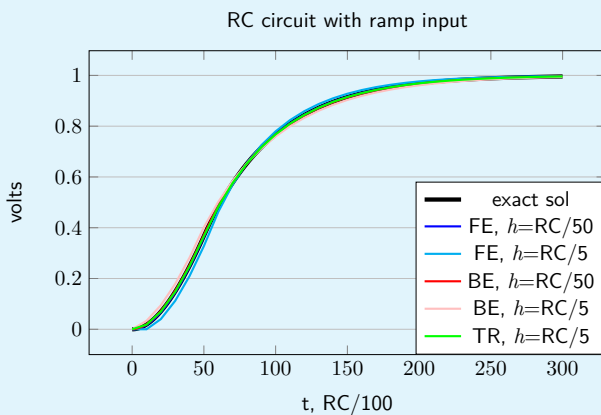

- For RC network with ramp input, trapezoidal rule is still more accurate than Forward Euler or Backward Euler with larger time steps.

## Nonlinear Dynamic Equation

- The diode capacitance is a nonlinear function of the voltage.

$$C_d = C_J \left(1 - \frac{V_d}{\phi_B}\right)^{-M}, \quad V_d < 0,$$


$$= C_J \left(1 + \frac{MV_d}{\phi_B}\right), \quad V_d \geq 0.$$

$V_d$ : voltage across diode,

$C_J$ : junction capacitance at  $V_d = 0$  volts,

$M$ : junction grading coefficient,

$\phi_B$ : junction contact potential.

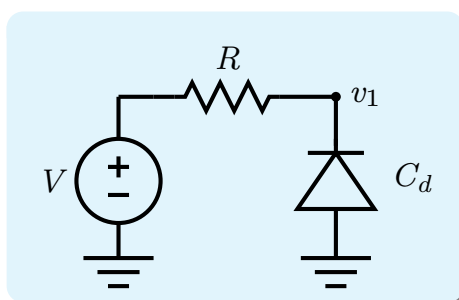


$$R = 50 \text{ K}\Omega,$$

$$C_J = 1 \text{ pF},$$

$$M = 0.5,$$


$$\phi_B = 0.8.$$

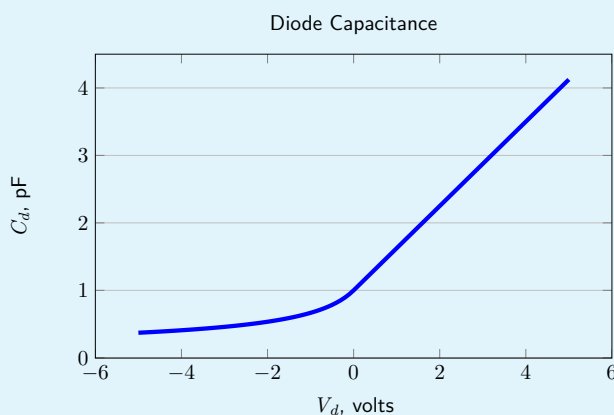


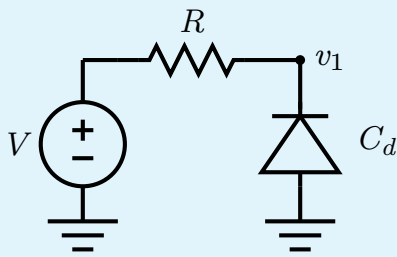
# Nonlinear Dynamic Equation, II

- Ignoring diode off current for the time being
- Nodal equation for  $v_1$



$$C_d \frac{dv_1}{dt} + \frac{v_1 - V}{R} = 0$$

$$\frac{dv_1}{dt} = \frac{V - v_1}{RC_d}$$

- Apply forward Euler method



$$\frac{v_1(t+h) - v_1(t)}{h} = \frac{V(t) - v_1(t)}{RC_d(-v_1(t))}$$

$$v_1(t+h) = v_1(t) + h \cdot \frac{V(t) - v_1(t)}{RC_d(-v_1(t))}$$

$R = 50 \text{ K}\Omega$ ,  
 $C_J = 1 \text{ pF}$ ,  
 $M = 0.5$ ,  
 $\phi_B = 0.8$ ,  
 $V(t) = 1, \quad t \geq 0$ ,  
 $v_1(0) = 0 \text{ volts}$ .

- The same equation as the linear cap case, except  $C_d$  is a function of  $v_1$  now
- Since the right-hand side is evaluated at time  $t$ ,  $v_1(t+h)$  can be easily calculated.
- The advantage of forward Euler method.

# Nonlinear Dynamic Equation, III

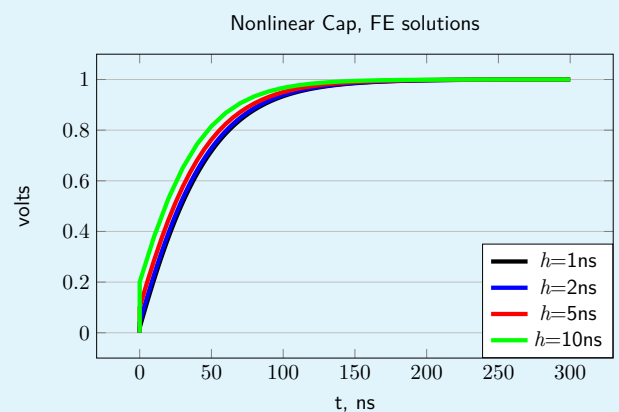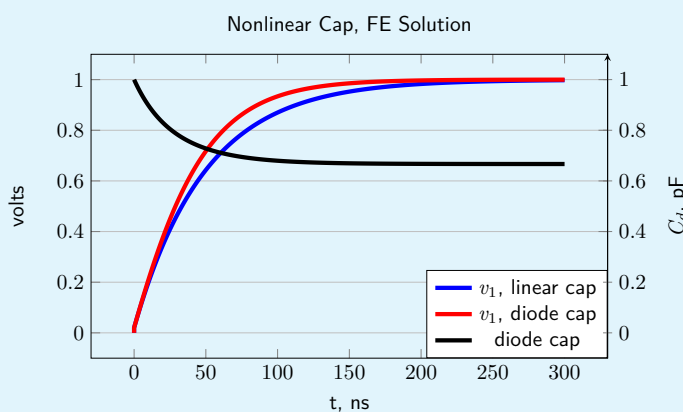

- Forward Euler method is effective in solving nonlinear dynamic equation.
- Since diode is in reverse bias region, the capacitance decreases and faster voltage ramp up is observed.
- Different time steps can still be exploited for speed-accuracy trade off.

# NDE, Backward Euler Solution

- Nodal equation for  $v_1$

$$\frac{dv_1}{dt} = \frac{V - v_1}{RC_d}$$

- Backward Euler method:

$$\frac{v_1(t+h) - v_1(t)}{h} = \frac{V(t+h) - v_1(t+h)}{RC_d},$$

$$\left(1 + \frac{h}{RC_d}\right)v_1(t+h) - v_1(t) - \frac{h}{RC_d}V(t+h) = 0. \quad (8.1.7)$$

This equation is nonlinear and can be solved by Newton's method.

$$v_1^{(k+1)}(t+h) = v_1^{(k)}(t+h) - \frac{f(v_1(t+h))}{df(v_1(t+h))/dv_1(t+h)}. \quad (8.1.8)$$

$$\begin{aligned} R &= 50 \text{ K}\Omega, \\ C_J &= 1 \text{ pF}, \\ M &= 0.5, \\ \phi_B &= 0.8, \\ V(t) &= 1, \quad t \geq 0, \\ v_1(0) &= 0 \text{ volts.} \end{aligned}$$

## NDE, Backward Euler Solution, II



- In Eq. (8.1.8)

$$f(v_1(t+h)) = \left(1 + \frac{h}{RC_d}\right)v_1(t+h) - v_1(t) - \frac{h}{RC_d}V(t+h), \quad (8.1.9)$$

and

$$\frac{df(v_1(t+h))}{dv_1(t+h)} = 1 + \frac{h}{RC_d}, \quad (8.1.10)$$

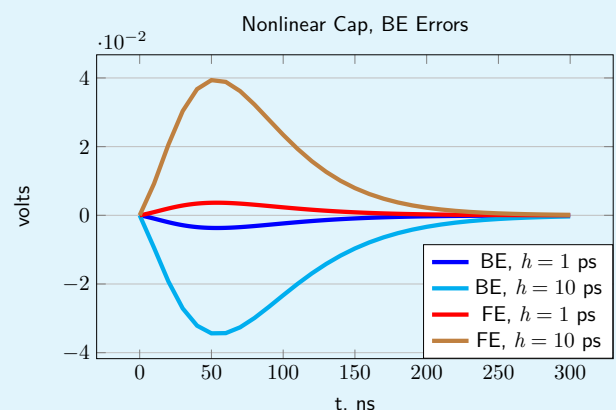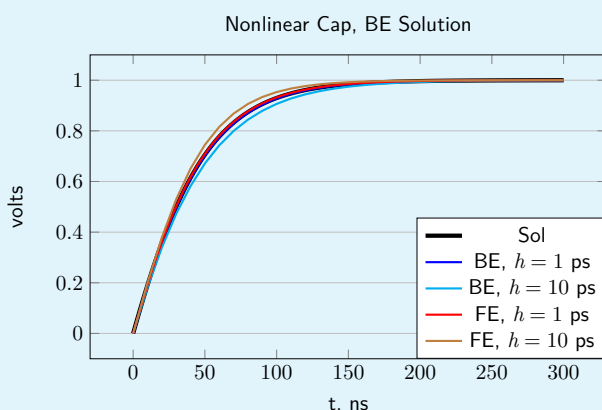where  $C_d$  should be evaluated at  $v_1(t+h)$ .



# NDE, Trapezoidal Rule Solution

- Apply trapezoidal rule to the nodal equation of the nonlinear diode capacitor circuit

$$\frac{v_1(t+h) - v_1(t)}{h} = \frac{V(t+h) - v_1(t+h)}{2RC_d(t+h)} + \frac{V(t) - v_1(t)}{2RC_d(t)}.$$

Again, apply Newton's method to solve this nonlinear equation with



$$f(v_1(t+h)) = \left(1 + \frac{h}{2RC_d(t+h)}\right)v_1(t+h) - \left(1 - \frac{h}{2RC_d(t)}\right)v_1(t) - \frac{h}{2RC_d(t+h)}V(t+h) - \frac{h}{2RC_d(t)}V(t),$$

$$\frac{df(v_1(t+h))}{dv_1(t+h)} = 1 + \frac{h}{2RC_d(t+h)}.$$

and iterate

$$v_1^{(k+1)}(t+h) = v_1^{(k)}(t+h) - \left(\frac{df(v_1(t+h))}{dv_1(t+h)}\right)^{-1} f(v_1(t+h)).$$


## NDE, Trapezoidal Rule Solution, II

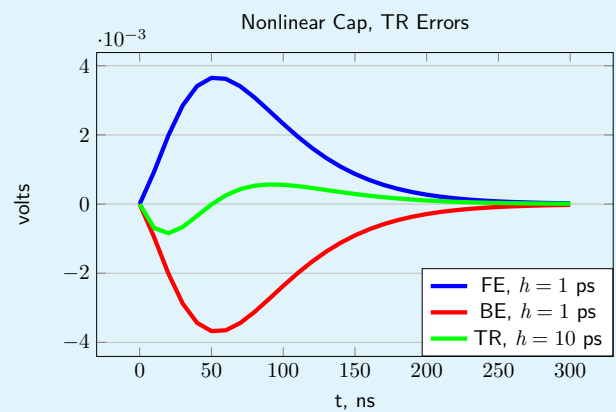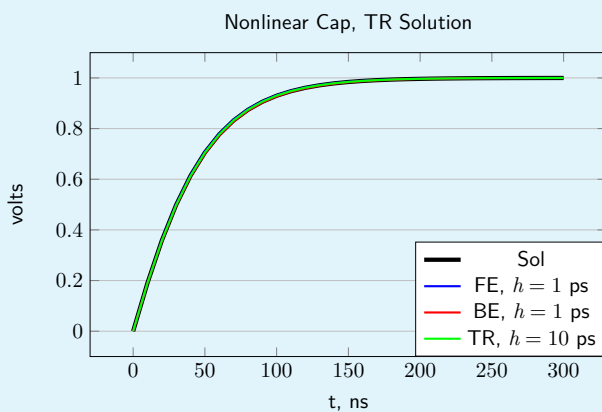

- Nonlinear dynamic equations can be solved using Newton's method and forward Euler, backward Euler or trapezoidal rule
- Trapezoidal rule has more complex formulation but with higher accurate solutions.
  - Higher accuracy with the same time step,
  - Or, with similar accuracy but larger time steps
- Newton's method needs good initial guess
  - In solving time point  $t+h$ , the solutions at  $t$  can be used as initial guess.
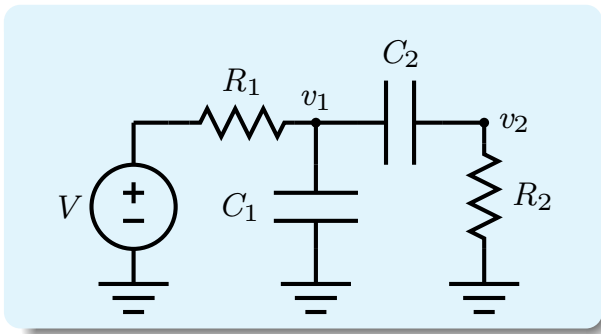
# Solving Dynamic Systems

- The forward Euler, backward Euler and trapezoidal rule methods can be applied to dynamic systems that have more than one variables.
- For example a two-stage RC ladder network.



- Given initial conditions:  $v_1(0)$ ,  $v_2(0)$  and power supply  $V(t)$ , for  $t \geq 0$ , to find  $v_1(t)$ ,  $v_2(t)$ ,  $t > 0$ .
- This linear dynamic system can be solved using any of the integration methods developed above.
- Applying KCL at node  $v_2$

$$C_2 \frac{d(v_2 - v_1)}{dt} + \frac{v_2}{R_2} = 0. \quad (8.1.11)$$

Using backward Euler method and assuming we know  $v_1(t)$  and  $v_2(t)$  to solve for  $v_1(t+h)$ ,  $v_2(t+h)$ .

## Solving Dynamic Systems, II

- Backward Euler approximates  $\frac{dx}{dt} = f(x, t)$  by

$$\frac{x(t+h) - x(t)}{h} = f(x(t+h), t+h).$$

- Eq. (8.1.11) can be rewritten as

$$\frac{C_2}{h} (v_2(t+h) - v_1(t+h) - v_2(t) + v_1(t)) + \frac{v_2(t+h)}{R_2} = 0.$$

Since  $v_1(t)$  and  $v_2(t)$  are already known, it can be rewritten as

$$\frac{C_2}{h} (v_2(t+h) - v_1(t+h)) + \frac{v_2(t+h)}{R_2} = \frac{C_2}{h} (v_2(t) - v_1(t)). \quad (8.1.12)$$

- Similarly for  $v_1$

$$\frac{v_1 - V}{R_1} + C_1 \frac{dv_1}{dt} + C_2 \frac{d(v_1 - v_2)}{dt} = 0.$$

And, with backward Euler

$$\frac{v_1(t+h) - V(t+h)}{R_1} + \frac{C_1}{h} v_1(t+h) + \frac{C_2}{h} (v_1(t+h) - v_2(t+h)) \quad (8.1.13)$$

$$= \frac{C_1}{h} v_1(t) + \frac{C_2}{h} (v_1(t) - v_2(t)). \quad (8.1.14)$$

## Solving Dynamic Systems, III

- Merging Eqs (8.1.12) and (8.1.14) and arrange in matrix-vector form

$$\begin{bmatrix} \frac{1}{R_1} + \frac{C_1}{h} + \frac{C_2}{h} & -\frac{C_2}{h} \\ -\frac{C_2}{h} & \frac{1}{R_2} + \frac{C_2}{h} \end{bmatrix} \begin{bmatrix} v_1(t+h) \\ v_2(t+h) \end{bmatrix} = \begin{bmatrix} \frac{C_1}{h} v_1(t) + \frac{C_2}{h} (v_1(t) - v_2(t)) \\ \frac{C_2}{h} (v_2(t) - v_1(t)) \end{bmatrix} \quad (8.1.15)$$

- Note that the stamps for a resistor,  $R_k$ , connecting nodes  $i$  and  $j$  are

$$A_{ii} = A_{ii} + \frac{1}{R_k}, \quad A_{ij} = A_{ij} - \frac{1}{R_k}, \quad A_{jj} = A_{jj} + \frac{1}{R_k}, \quad A_{ji} = A_{ji} - \frac{1}{R_k}. \quad (8.1.16)$$

- In a similar way, we can define the stamps for a capacitor,  $C_k$ , connect nodes,  $i$  and  $j$ , to be

$$\begin{aligned} A_{ii} &= A_{ii} + \frac{C_k}{h}, & A_{ij} &= A_{ij} - \frac{C_k}{h}, & b_i &= b_i + \frac{C_k}{h} (v_i(t) - v_j(t)), \\ A_{jj} &= A_{jj} + \frac{C_k}{h}, & A_{ji} &= A_{ji} - \frac{C_k}{h}, & b_j &= b_j + \frac{C_k}{h} (v_j(t) - v_i(t)). \end{aligned} \quad (8.1.17)$$

when the backward Euler method is used to solve the circuit.

- Using stamping method, we can formulate and simulate RC circuit effectively.

## Solving Dynamic Systems, IV

- When using backward Euler method to solve the dynamic circuits, the stamps of a capacitor,  $C_k$ , connecting nodes  $i$  and  $j$ , can also be derived as the following.
- KCL requires the total current leaving a node to be zero. And the current of the capacitor is

$$C_k \frac{d(v_i - v_j)}{dt} = I_c$$

Using the backward Euler method

$$\begin{aligned} C_k \frac{v_i(t+h) - v_j(t+h) - v_i(t) + v_j(t)}{h} &= I_c(t+h) \\ \frac{C_k}{h} (v_i(t+h) - v_j(t+h) - v_i(t) + v_j(t)) &= I_c(t+h) \end{aligned}$$

Since  $\frac{C_k}{h} (v_i(t) - v_j(t))$  is a known quantity, it should be added to the right-hand side of the equation. Thus, the stamps are

$$\begin{aligned} A_{ii} &= A_{ii} + \frac{C_k}{h} & A_{ij} &= A_{ij} - \frac{C_k}{h} & b_i &= b_i + \frac{C_k}{h} (v_i(t) - v_j(t)) \\ A_{jj} &= A_{jj} + \frac{C_k}{h} & A_{ji} &= A_{ji} - \frac{C_k}{h} & b_j &= b_j + \frac{C_k}{h} (v_j(t) - v_i(t)) \end{aligned}$$

# Solving Dynamic Systems, V

- The forward Euler method, which does not have  $I_c(t+h)$  term in the formula and, thus, cannot formulate stamps.
- If the trapezoidal rule is applied, Eq. (8.1.11) should be written as

$$C_k \frac{v_i(t+h) - v_j(t+h) - v_i(t) + v_j(t)}{h} = \frac{I_c(t+h) + I_c(t)}{2}$$

And, thus the current through the capacitor at time  $t+h$  is

$$I_c(t+h) = \frac{2C_k}{h} (v_i(t+h) - v_j(t+h) - v_i(t) + v_j(t)) - I_c(t). \quad (8.1.18)$$

This current should be added to the matrix equation, and thus the stamps are

$$\begin{aligned} A_{ii} &= A_{ii} + \frac{2C_k}{h} & A_{ij} &= A_{ij} - \frac{2C_k}{h} & b_i &= b_i + \frac{2C_k}{h} (v_i(t) - v_j(t)) + I_c(t) \\ A_{jj} &= A_{jj} + \frac{2C_k}{h} & A_{ji} &= A_{ji} - \frac{2C_k}{h} & b_j &= b_j + \frac{2C_k}{h} (v_j(t) - v_i(t)) + I_c(t) \end{aligned} \quad (8.1.19)$$

where  $I(t)$  is the current through the capacitor at time  $t$ .

- When using trapezoidal rule, the capacitor current of the previous time step needs to be used and it can be calculated using Eq. (8.1.18).
- At  $t=0$ , DC condition is assumed and  $I_c(0) = 0$ .

## Theoretical Results

- It is assumed

$$\mathbf{x}' = f(t, \mathbf{x}) \quad (8.1.20)$$

is a system of  $n$  ordinary differential equations, and

$$\mathbf{x}(t_0) = \mathbf{x}_0. \quad (8.1.21)$$

### Theorem 8.1.1.

Let  $f$  be defined and continuous on  $\mathbf{S} = \{(t, \mathbf{x}), a \leq t \leq b, \mathbf{x} \in \mathbb{R}^n\}$ ,  $a$  and  $b$  are finite. Furthermore, let there be a constant  $L$  such that

$$\|f(t, \mathbf{x}_1) - f(t, \mathbf{x}_2)\| \leq L \|\mathbf{x}_1 - \mathbf{x}_2\| \quad (8.1.22)$$

for all  $t \in [a, b]$  and all  $\mathbf{x}_1, \mathbf{x}_2 \in \mathbb{R}^n$  (Lipschitz condition). Then for every  $t_0 \in [a, b]$  and every  $\mathbf{x}_0 \in \mathbb{R}^n$  there is exactly one function  $\mathbf{x}(t)$  such that

- (a)  $\mathbf{x}(t)$  is continuous and continuously differentiable for  $t \in [a, b]$ ;
- (b)  $\mathbf{x}'(t) = f(t, \mathbf{x}(t))$  for  $t \in [a, b]$ ;
- (c)  $\mathbf{x}(t_0) = \mathbf{x}_0$ .

## Theoretical Results, II

### Theorem 8.1.2.

Let the function  $f: S \rightarrow \mathbb{R}^n$  be continuous on  $S = \{(t, \mathbf{x}), a \leq t \leq b, \mathbf{x} \in \mathbb{R}^n\}$  and satisfy the Lipschitz condition

$$\|f(t, \mathbf{x}_1) - f(t, \mathbf{x}_2)\| \leq L\|\mathbf{x}_1 - \mathbf{x}_2\|$$

for all  $(t, \mathbf{x}_1), (t, \mathbf{x}_2) \in S$ . Let  $a \leq t_0 \leq b$ . Then for the solution  $\mathbf{X}(t, \mathbf{s})$  of the initial value problem

$$\mathbf{x}' = f(t, \mathbf{x}), \quad \mathbf{x}(t_0, \mathbf{s}) = \mathbf{s} \quad (8.1.23)$$

there holds the estimate

$$\|\mathbf{x}(t, \mathbf{s}_1) - \mathbf{x}(t, \mathbf{s}_2)\| \leq e^{L|t-t_0|} \|\mathbf{s}_1 - \mathbf{s}_2\| \quad (8.1.24)$$

for  $a \leq t \leq b$ .

## Theoretical Results, III

### Theorem 8.1.3.

If in addition to assumption of the preceding theorem the Jacobian matrix  $\mathbf{J}_x = [\partial f_i / \partial x_j]$  exists on  $S$  and is continuous and bounded,

$$\|\mathbf{J}_x\| \leq L \quad \text{for } (t, \mathbf{x}) \in S,$$

then the solution  $\mathbf{x}(t, \mathbf{s})$  of  $\mathbf{x}' = f(t, \mathbf{x})$ ,  $\mathbf{x}(t_0, \mathbf{s}) = \mathbf{s}$ , is continuously differentiable for all  $t \in [a, b]$  and all  $\mathbf{s} \in \mathbb{R}^n$ . The derivative

$$\mathbf{Z}(t, \mathbf{x}) = [\partial x_i(t, \mathbf{s}) / \partial s_j], \quad (8.1.25)$$

is the solution of the initial value problem

$$\mathbf{Z}' = \mathbf{J}_x \mathbf{Z}, \quad \mathbf{Z}(t_0, \mathbf{s}) = \mathbf{I}. \quad (8.1.26)$$

Note that all entities in Eq. (8.1.26) are  $n \times n$  matrices, and can be obtained by differentiating with respect to  $\mathbf{s}$  the original system of equations.

$$\mathbf{x}' = f(t, \mathbf{x}(t, \mathbf{s})), \quad \mathbf{x}(t_0, \mathbf{s}) = \mathbf{s}.$$

- Suppose Eq. (8.1.26) is rewritten as

$$\mathbf{Z}' = \mathbf{T}(t)\mathbf{Z}, \quad \mathbf{Z}(a) = \mathbf{I}. \quad (8.1.27)$$

## Theorem 8.1.4.

If  $\mathbf{T}(t)$  is continuous on  $[a, b]$ , and let  $k(t) = \|\mathbf{T}(t)\|$ , then the solution  $\mathbf{Z}(t)$  of Eq. (8.1.27) satisfies

$$\|\mathbf{Z}(t) - \mathbf{I}\| \leq \exp\left(\int_a^b k(t) dt\right) - 1, \quad t \geq a. \quad (8.1.28)$$

- This is the extended version of Theorem (8.1.2).
- The solution of the initial value problem depends on the initial condition and grows exponentially with the independent variable  $t$ .

## Summary

- Ordinary differential equation
  - Initial value problem
- Forward Euler Method
  - RC network example
- Backward Euler method
  - RC network with ramp input
- Trapezoidal rule
- Nonlinear dynamic equations
- Capacitor stamps
  - Backward Euler method
  - Trapezoidal rule method