


# Numerical Analysis

## Homework 4. Resistor Networks


**Due: March 31, 2015**

Please formulate and solve the following resistor network problems.

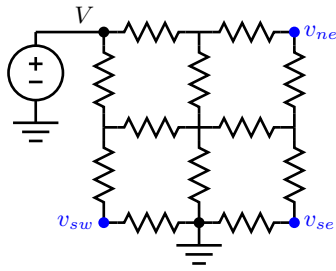
1. Assuming each resistor is  $1\text{ K}\Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{sw}$  and  $v_{se}$ .



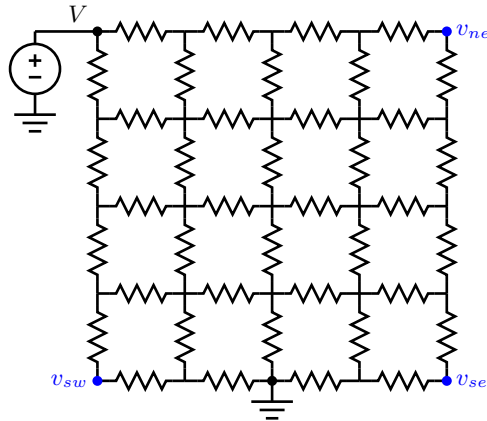
2. Assuming each resistor is  $500\text{ }\Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{sw}$  and  $v_{se}$ .



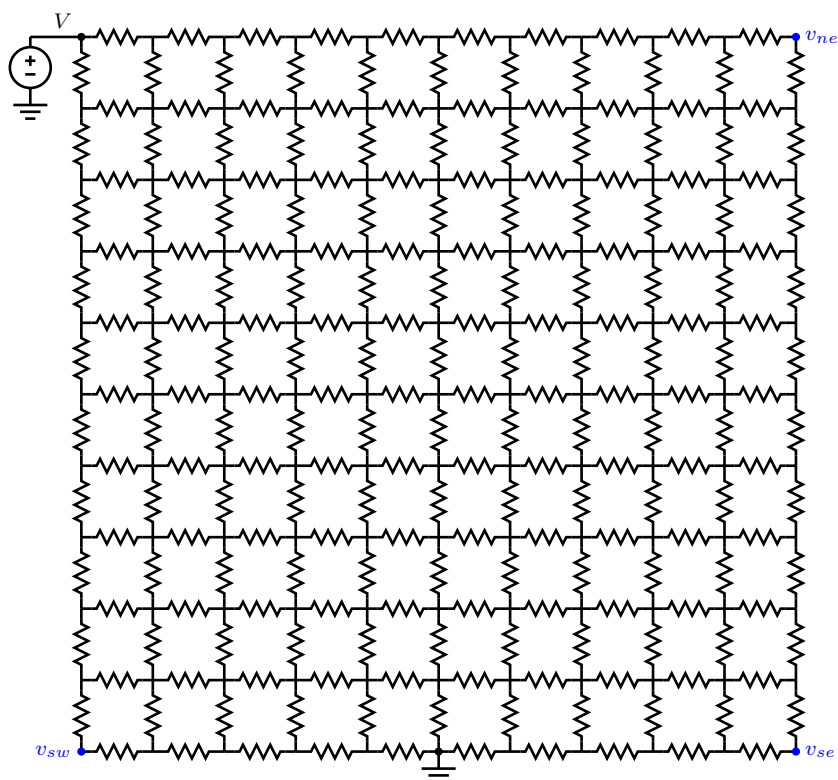3. Assuming each resistor is  $200\ \Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{sw}$  and  $v_{se}$ .



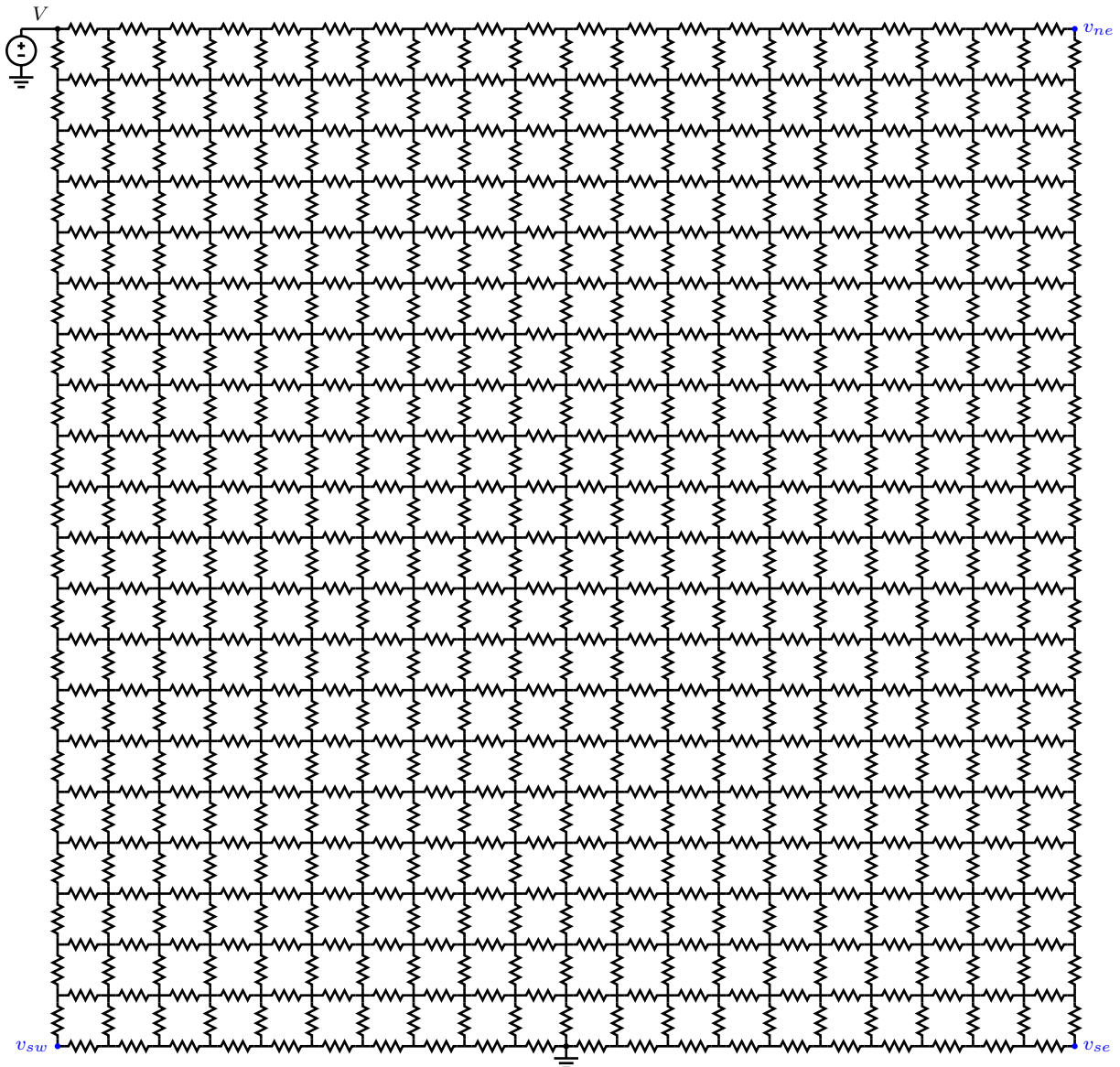4. Assuming each resistor is  $100\ \Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{sw}$  and  $v_{se}$ .



5. Please state your observations after solving all four questions.

### Notes.

1. For this homework you need to turn in a **C++** program that solves the resistor network problem for question 4. If your program is parametrized then it can solve for all 4 problems using command line arguments. For example,

```
$ ./a.out 10
```

to solve question 3 that each linear dimension has 10 resistors. If your program is not parametrized, then turn in the one that solves question 4. Name your program `hw04.cpp`.

2. A pdf file is also needed. Please name this file `hw04a.pdf`.

3. Submit your files on EE workstations. Please use the following command to submit your homework 4.

```
$ ~ee407002/bin/submit hw04 hw04a.pdf hw04.cpp MAT.h MAT.cpp VEC.h VEC.cpp
```

where **hw04** indicates homework 4.

4. Your report should be clearly written such that I can understand it. The writing, including English grammar, is part of the grading criteria.